

Arianna Banton

The screenshots have one LED light, a bread board, 3 AA 1.5V batteries and a 330K resistor. The battery is connected to the bread board by a positive a negative wire. Allowing an electrical charge to run through the bread board. There are also two separate positive and negative wires connecting both side of the bread boards. The LED light has a anode and a cathode the cathode has a negative energy running though it by me connecting a wire from the negative side to the row/column 23a. the anode is on the same column as terminal 2 on the resistor. Terminal 1 is receiving positive power from a wire connecting the positive side to the row/column 28b. With everything in place the light turns on when the simulation is started.


lab 2 Electronics

TINKERCAD

lab 2 Electronics

Start Simulation

Code

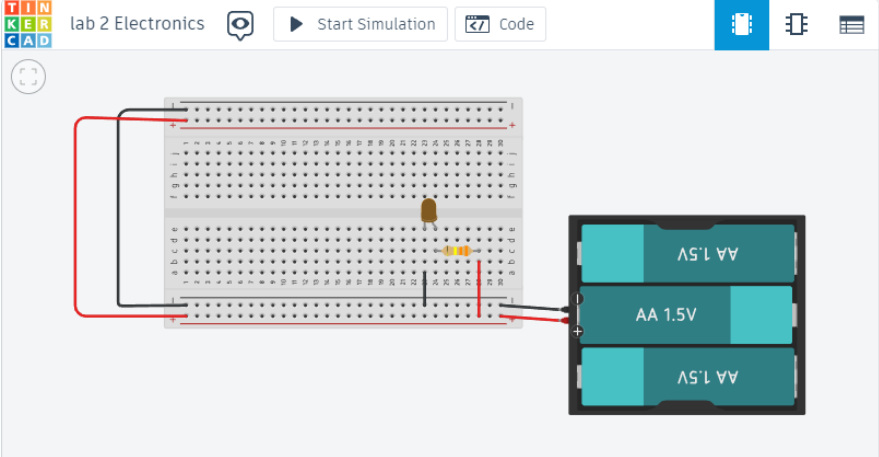

Circuit by

Arianna Banton

Tinker this

Share to Classroom

Copy link

Design is visible only to you.

[Change visibility to share](#)


Edited February 07, 2024

Created February 07, 2024

Above photo: light off

lab 2 Electronics

React  0

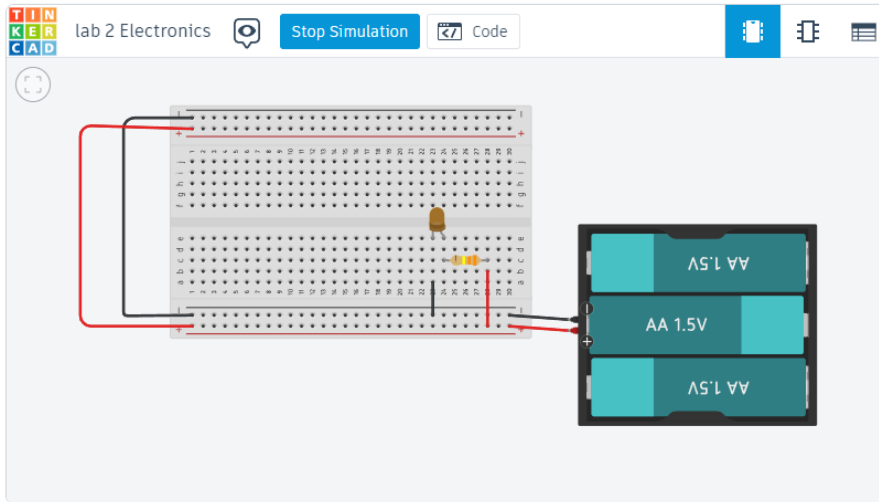

Circuit by
Arianna Banton

Tinker this

 **Share to Classroom**

Copy link

Design is visible only to you.

[Change visibility to share](#)


Edited February 07, 2024

Created February 07, 2024



 **Report content**

Above photo: light on

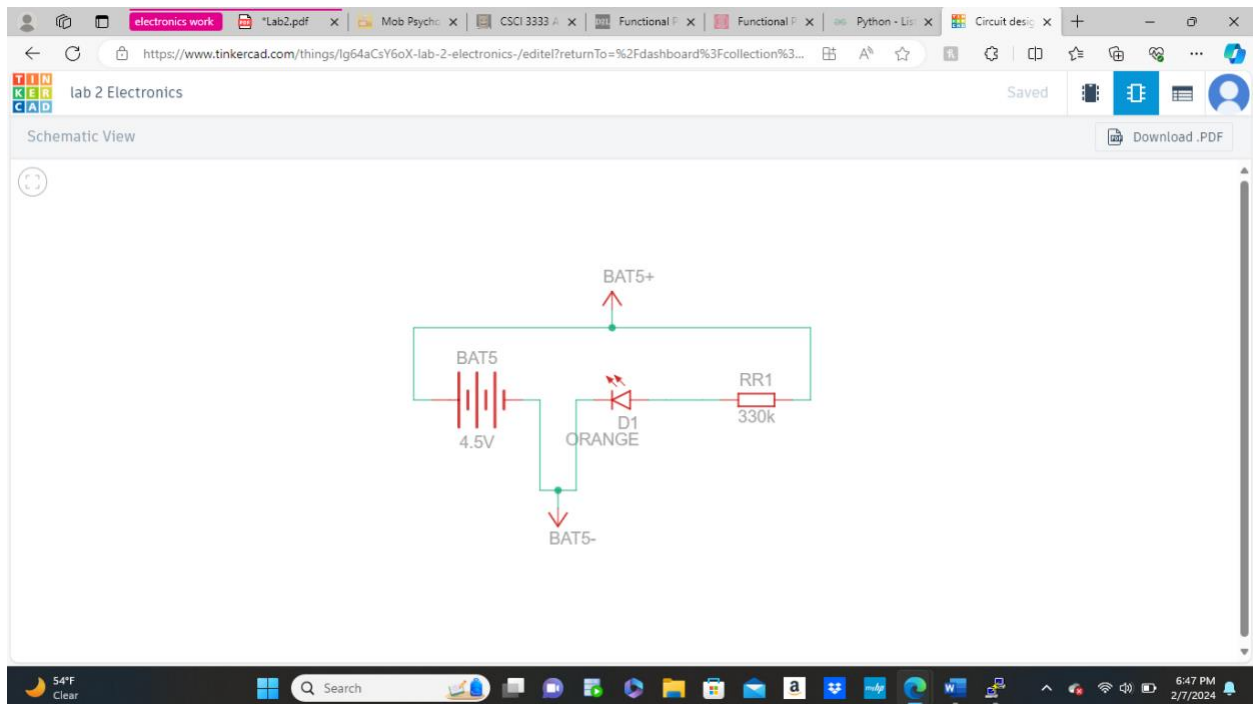

Above photo: schematic